

# Thevenin and Norton's Theorems

Aditya Arora

Winter 2018

April 12, 2018

## STATEMENTS

### A Statement of Thevenins Theorem

1. Given any linear circuit, rearrange it in the form of two networks, A and B, connected by two wires. Network A is the network to be simplified; B will be left untouched.
2. Disconnect network B. Define a voltage  $v_{oc}$  as the voltage now appearing across the terminals of network A.
3. Turn off or zero out every independent source in network A to form an inactive network. Leave dependent sources unchanged.
4. Connect an independent voltage source with value  $v_{oc}$  in series with the inactive network. Do not complete the circuit; leave the two terminals disconnected.
5. Connect network B to the terminals of the new network A. All currents and voltages in B will remain unchanged.

**CASE 1:** If the network has no dependent sources, we turn off all the independent sources.

**CASE 2:** If the network has dependent sources we turn off all independent sources. We can either then choose to apply a 1V source or a 1A source across the terminals and find  $R_{th}$  accordingly using the help of other circuit theorems

## A Statement of Nortons Theorem

1. Given any linear circuit, rearrange it in the form of two networks, A and B, connected by two wires. Network A is the network to be simplified; B will be left untouched. As before, if either network contains a dependent source, its controlling variable must be in the same network.
2. Disconnect network B, and short the terminals of A. Define a current  $i_{sc}$  as the current now flowing through the shorted terminals of network A.
3. Turn off or zero out every independent source in network A to form an inactive network. Leave dependent sources unchanged.
4. Connect an independent current source with value  $i_{sc}$  in parallel with the inactive network. Do not complete the circuit; leave the two terminals disconnected.
5. Connect network B to the terminals of the new network A. All currents and voltages in B will remain unchanged.

We can find any two of the following three to determine the Norton equivalent of a circuit:

1. The open-circuit voltage  $v_{oc}$  across terminals  $a$  and  $b$  (no current flows out from this open circuit)
2. The short-circuit current  $i_{sc}$  at terminals  $a$  and  $b$
3. The equivalent or input resistance at terminals  $a$  and  $b$  when all the independent sources are turned off

Using these we can find the Norton's equivalent since:

$$I_N = i_{sc}, V_{Th} = v_{oc}, R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$